

T.C. Trakya University
Faculty of Engineering
Department of Electrical and Electronics Engineering
Assist. Prof. Işık İlber Sırmatel

EEM/EEE314 Automatic Control Systems

Exam-style questions with solutions

Part 1: Electrical systems


Abbreviations:

KVL: Kirchhoff's voltage law

KCL: Kirchhoff's current law

LHS: left-hand side (of the equation)

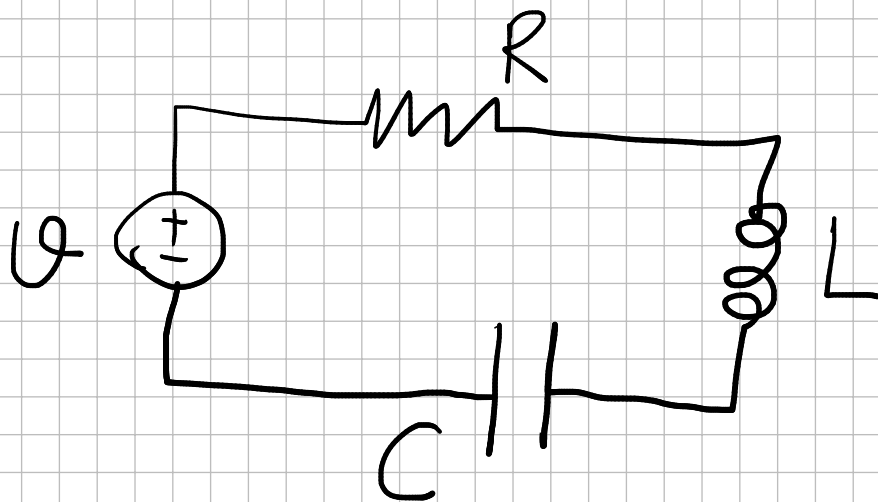Question 1: Consider the schematic of an electrical circuit depicted below, consisting of a resistor, an inductor, and a capacitor (with parameters R , L , and C , respectively). The charge accumulated on the capacitor is denoted as $q(t)$. An external voltage is applied to the circuit, denoted as $v(t)$. Find the differential equation model of the system relating $v(t)$ and $q(t)$.



Solution:

Denoting the voltage drops across the circuit elements as V_R , V_L , and V_C , respectively, and invoking KVL, we write:

$$v = V_R + V_L + V_C$$

Denoting the current flowing through the circuit as $i(t)$, and using linear models of the circuit elements, we write:

$$V_R = R \cdot i \quad V_L = L \cdot \dot{i}$$

$$V_C = \frac{1}{C} q$$

Note that, for the capacitor, the following are true:

① $q = \int i \, dt$ (accumulation of charge)

(or, equivalently: $i = \dot{q}$)

② voltage drop across the capacitor:

$$V_C = \frac{1}{C} q = \frac{1}{C} \int i \, dt$$

(or, equivalently: $i = C \cdot \dot{V}_C$)

The question asks us to relate v and q , thus we need to rewrite V_R and V_L in terms of q (using $i = \dot{q}$):

$$V_R = R \cdot i = R \cdot \dot{q}$$


$$V_L = L \cdot \dot{i} = L \cdot \ddot{q}$$

Rewriting KVL with these, we find:


$$V = R \dot{q} + L \ddot{q} + \frac{1}{C} q$$



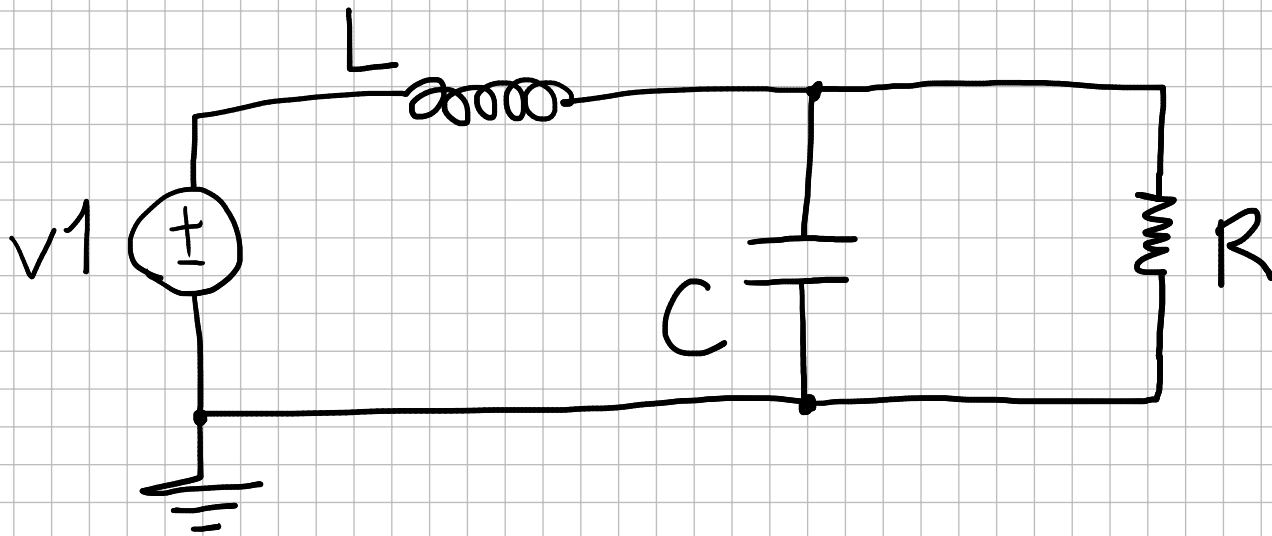Question 2: Consider the schematic of an electrical circuit depicted below, consisting of a resistor, an inductor, and a capacitor (with parameters R , L , and C , respectively). The voltage drop across the resistor is denoted as $v_2(t)$. An external voltage is applied to the circuit, denoted as $v_1(t)$. Find the differential equation model of the system relating $v_1(t)$ and $v_2(t)$.



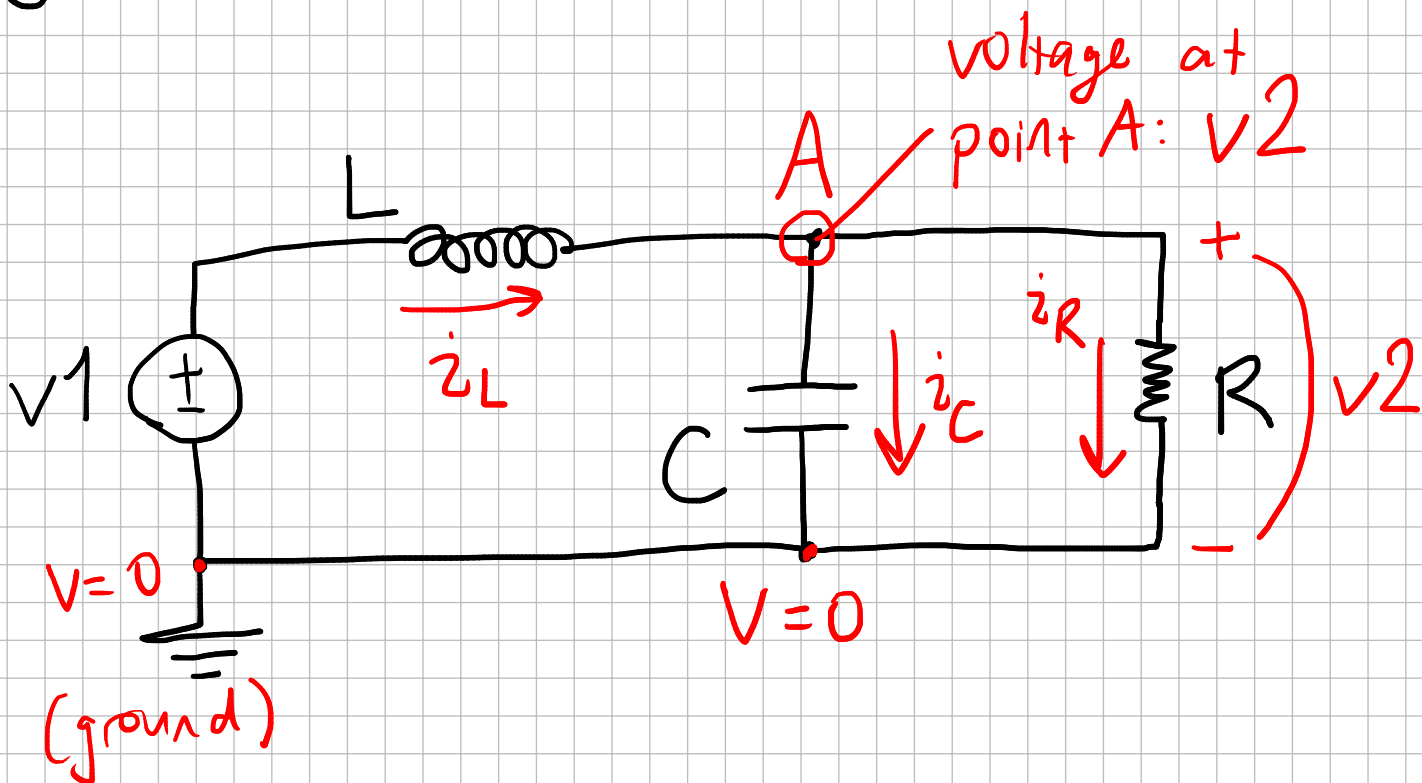Solution: Define the following symbols for the circuit:



Invoking KCL at point A:

$$i_L = i_C + i_R$$

Invoking KVL for left loop:

$$v_1 = V_L + v_2$$

The question asks us to relate v_1 and v_2 , thus we need to rewrite V_L and V_C in terms of v_2 .

Writing the linear model of the inductor: $V_L = L \cdot \dot{i}_L$

Rewriting KVL with this:

$$v_1 = L \cdot \dot{i}_L + v_2$$

We still need to rewrite i_L in terms of v_2 .

We found KCL for point A as follows: $i_L = i_C + i_R$

Differentiating both sides, we get: $\dot{i}_L = \dot{i}_C + \dot{i}_R$

From linear models of the capacitor and resistor, we can write:

$$i_C = C \cdot \dot{v}_2 \quad i_R = \frac{1}{R} v_2$$

Differentiating both:

$$\dot{i}_C = C \cdot \ddot{v}_2 \quad \dot{i}_R = \frac{1}{R} \cdot \dot{v}_2$$

Rewriting $\dot{i}_L = \dot{i}_C + \dot{i}_R$

with these, we have:

$$\dot{i}_L = C \cdot \ddot{v}_2 + \frac{1}{R} \cdot \dot{v}_2$$


Substituting this in the KVL:

$$v_1 = L \cdot \dot{i}_L + v_2$$


$$v_1 = L \cdot \left(C \cdot \ddot{v}_2 + \frac{1}{R} \dot{v}_2 \right) + v_2$$

$$v_1 = L \cdot C \cdot \ddot{v}_2 + \frac{L}{R} \cdot \dot{v}_2 + v_2$$

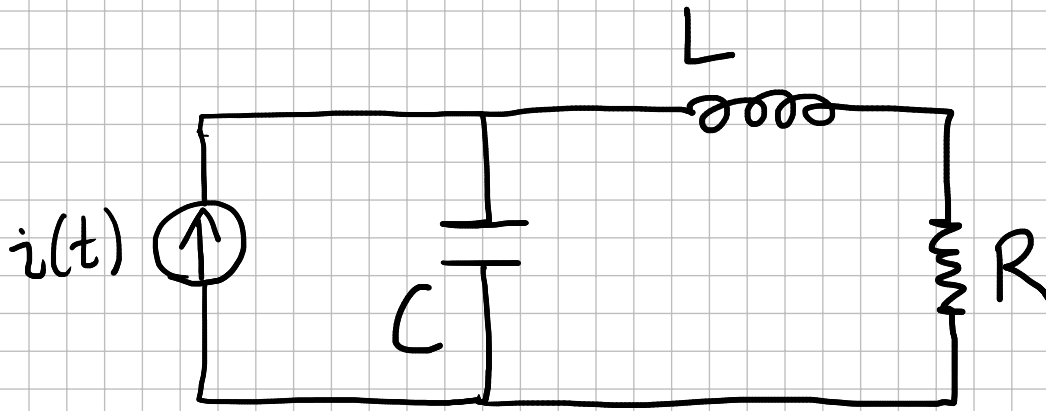Question 3: Consider the schematic of an electrical circuit depicted below, consisting of a resistor, an inductor, and a capacitor (with parameters R , L , and C , respectively). The current flowing through the inductor is denoted as $i_L(t)$. An external current is supplied to the circuit, denoted as $i(t)$. Find the differential equation model of the system relating $i(t)$ and $i_L(t)$.



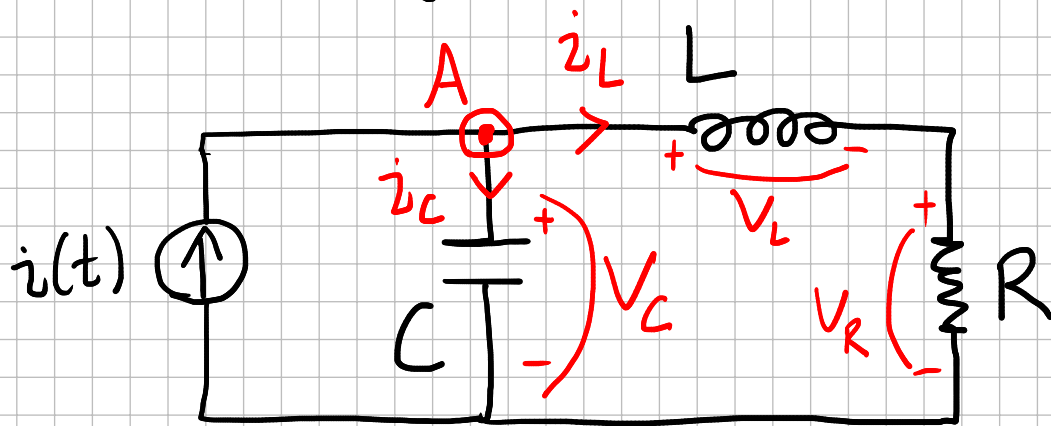Solution: Define the following symbols for the circuit:



Invoking KCL at point A:

$$\dot{i} = \dot{i}_C + \dot{i}_L$$

Invoking KVL for right loop:

$$V_C = V_L + V_R$$

From linear models of the inductor and the resistor, we can write:

$$V_L = L \cdot \dot{i}_L \quad V_R = R \cdot i_L$$

Rewriting KVL with these:

$$V_C = L \cdot \dot{i}_L + R \cdot i_L$$

Differentiating both sides:

$$\dot{V}_C = L \cdot \ddot{i}_L + R \cdot \dot{i}_L$$

Multiplying both sides by C :

$$[C \cdot \dot{V}_C = L \cdot C \cdot \ddot{i}_L + R \cdot C \cdot \dot{i}_L]$$

From linear model of the capacitor: $i_C = C \cdot \dot{V}_C$

→ This equation thus becomes:

$$[i_C = L \cdot C \cdot \ddot{i}_L + R \cdot C \cdot \dot{i}_L]$$

From KCL at point A we found:

$$i = i_C + i_L, \text{ thus: } i_C = i - i_L$$

Substituting i_C , this equation becomes:

$$i - i_L = L \cdot C \cdot \ddot{i}_L + R \cdot C \cdot \dot{i}_L$$

rearranging to have i_L terms on LHS:

$$LC \ddot{i}_L + RC \dot{i}_L + i_L = i$$